

Solutions to Classwork #10 #15

Diagnosis + Compression

Team: _____ Name: _____ Score: _____ Reviewer: _____


CW 每次一小時，總共六十分，互相交換改。

各題批改標準：方法對答案錯一處扣該題總分 20% (同一原因扣一次)。方法錯一處扣 60%。有爭議給助教改。

Each CW has 60 points in total. Answer time is one hour. Swap your test sheet with others for grading purposes.

Grading criteria for each problem: if an answer is wrong but the method is correct, 20% of the total score of this problem will be deducted (Multiple wrong answers with the same root cause are treated as one). 60% deduction for a wrong method. Ask the TAs if there are disputes about grading criteria.

Problem 1 Diagnosis <video 10.3> (15 points)

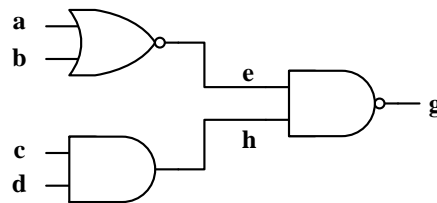Consider the following circuit and single stuck-at fault model. We apply 4 patterns $abcd = \{0111, 0011, 1001, 1011\}$. Consider only $a/0, c/1, e/1, h/0, g/0, g/1$.A. Assume the circuit fails the 4th test pattern. Please diagnose the circuit using **dynamic cause-effect diagnosis**. Show how you remove faults by the three rules.B. Show the partial fault dictionary with scores $10 \times \text{TF SF} - \text{TP SF}$. What's the diagnosed fault?

A. Please fill in the good values into the following table first.

pattern #	a	b	c	d	e	h	g
1	0	1	1	1	0	1	1
2	0	0	1	1	1	1	0
3	1	0	0	1	0	0	1
4	1	0	1	1	0	1	1

Step 1. Structural backtracing

Only one primary output, no faults can be eliminated

Step 2. Parity check

Example : $a/0: v = 0; p = 0; f = 0 \quad v \oplus p = 0$ fault remains $c/1: v = 1; p = 1; f = 0 \quad v \oplus p = 0$ fault remains $e/1: v = 1; p = 1; f = 0 \quad v \oplus p = 0$ fault remains $h/0: v = 0; p = 1; f = 0 \quad v \oplus p = 1$ fault eliminated $g/0: v = 0; p = 0; f = 0 \quad v \oplus p = 0$ fault remains $g/1: v = 1; p = 0; f = 0 \quad v \oplus p = 1$ fault eliminated

Step 3. Excitation condition check

 $c/1$ eliminated due to no excitation ($c = 1$ in the 4th pattern)

B. Please fill in the following table as your partial fault dictionary.

Fault	Pattern1	Pattern2	Pattern3	Pattern4	TF SF	TP SF	Score ($10 \times \text{TF SF} - \text{TP SF}$)
$a/0$				X	1	0	10
$e/1$	X			X	1	1	9
$g/0$	X		X	X	1	2	8
Test Failure				X			


The diagnosed single stuck-at fault is $a/0$

Solutions to Classwork #10 #15

Diagnosis + Compression

Problem 2 PODEM-X <video 15.1> (15 points)

Consider the following circuit.

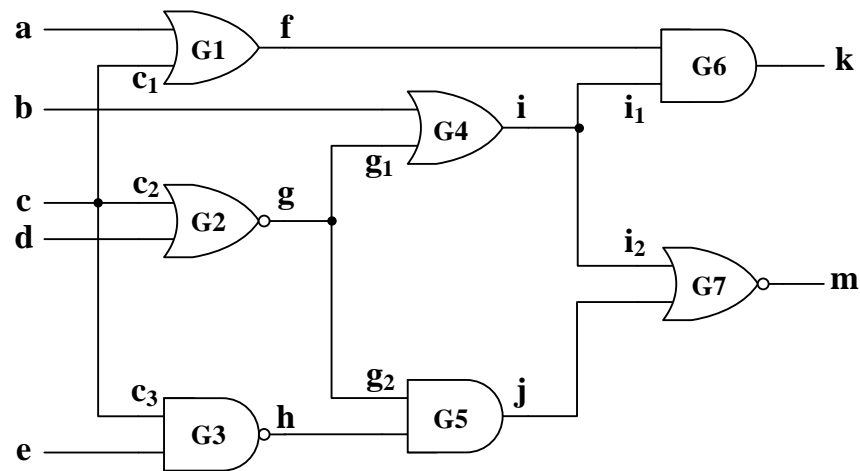

The primary fault is g SA0 fault and the secondary fault is f SA0.

Please generate a test pattern using PODEM-X algorithm. If the test doesn't exist, please explain.

Use level for easy/hard to control input when backtracing.

Primary Fault: g SA0

Initial objective: $g = 1$

Backtrace to PI: $c = 0$

Implication: $h = 1$

Backtrace to PI: $d = 0$


Implication: $g = g_1 = g_2 = D, j = D$

Objective: $i_2 = 0$

Backtrace to PI: $b = 0$

Implication: $i = i_1 = i_2 = D, m = D'$

Test cube: $abcde = x 0 0 0 x$

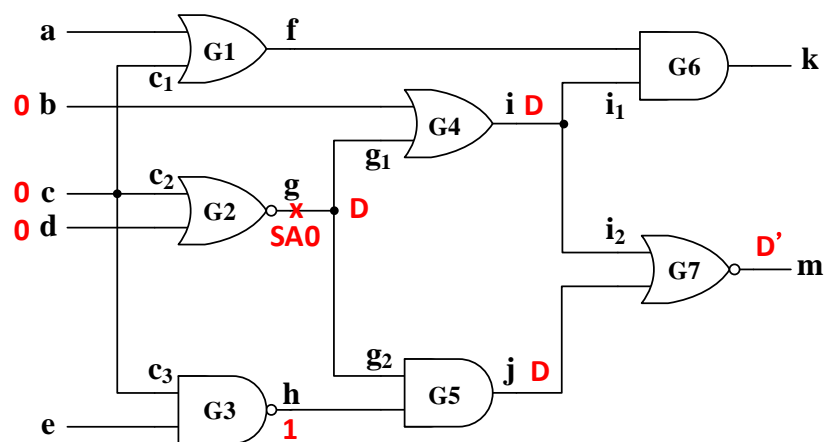

Solutions to Classwork #10 #15

Diagnosis + Compression

(change D to 1, D' to 0 due to single fault assumption)


Choose secondary fault = f SA0

Objective: $f = 1$

Backtrace to PI: $a = 1$

Implication: $f = D$, $k = D$, fault detected

New test cube: $abcde = 1\ 0\ 0\ 0\ x$

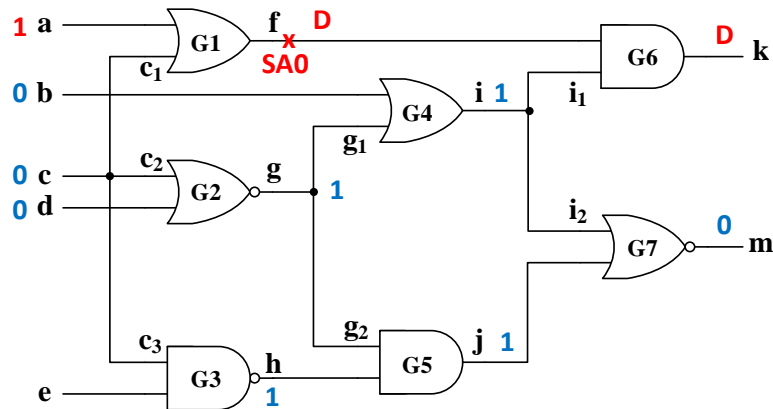

Problem 3 Static Test Compression<Video 15.2> (15 points)

Consider the following covering table (X = detection). Please answer

- Which are essential faults?
- Which are dominated rows?
- After remove dominated rows, which are dominating columns?
- What is minimum test set?
- List 01-ILP objective and all constraints (consider the original table)

	f_1	f_2	f_3	f_4	f_5
t_1	X		X		X
t_2		X	X		
t_3	X			X	
t_4	X	X	X		X

- f_4
- $t_1 \cdot t_2$
- f_1 is dominating column
- $t_3 \cdot t_4$
- $t_i = 1$ if test i is selected; $t_i = 0$ otherwise.

Objective: $\min t_1 + t_2 + t_3 + t_4$

Constraint1: $t_1 + t_3 + t_4 \geq 1$ (for f_1)

Constraint2: $t_2 + t_4 \geq 1$ (for f_2)

Constraint3: $t_1 + t_2 + t_4 \geq 1$ (for f_3)

Constraint4: $t_3 \geq 1$ (for f_4)

Constraint5: $t_1 + t_4 \geq 1$ (for f_5)


Solutions to Classwork #10 #15

Diagnosis + Compression

Problem 4 Tseng-Siewiorek Algorithm <video 15.2> (15 points)

For the following patterns, please use Tseng-Siewiorek Algorithm to find minimal test cube.

Pattern	
1	1 X 0 X X X
2	0 X 0 0 1 0
3	1 0 0 1 0 X
4	X 0 X 1 X 1
5	X 1 1 X 1 1
6	0 X X 1 0 X
7	X 1 0 1 0 0
8	1 X 1 0 X X

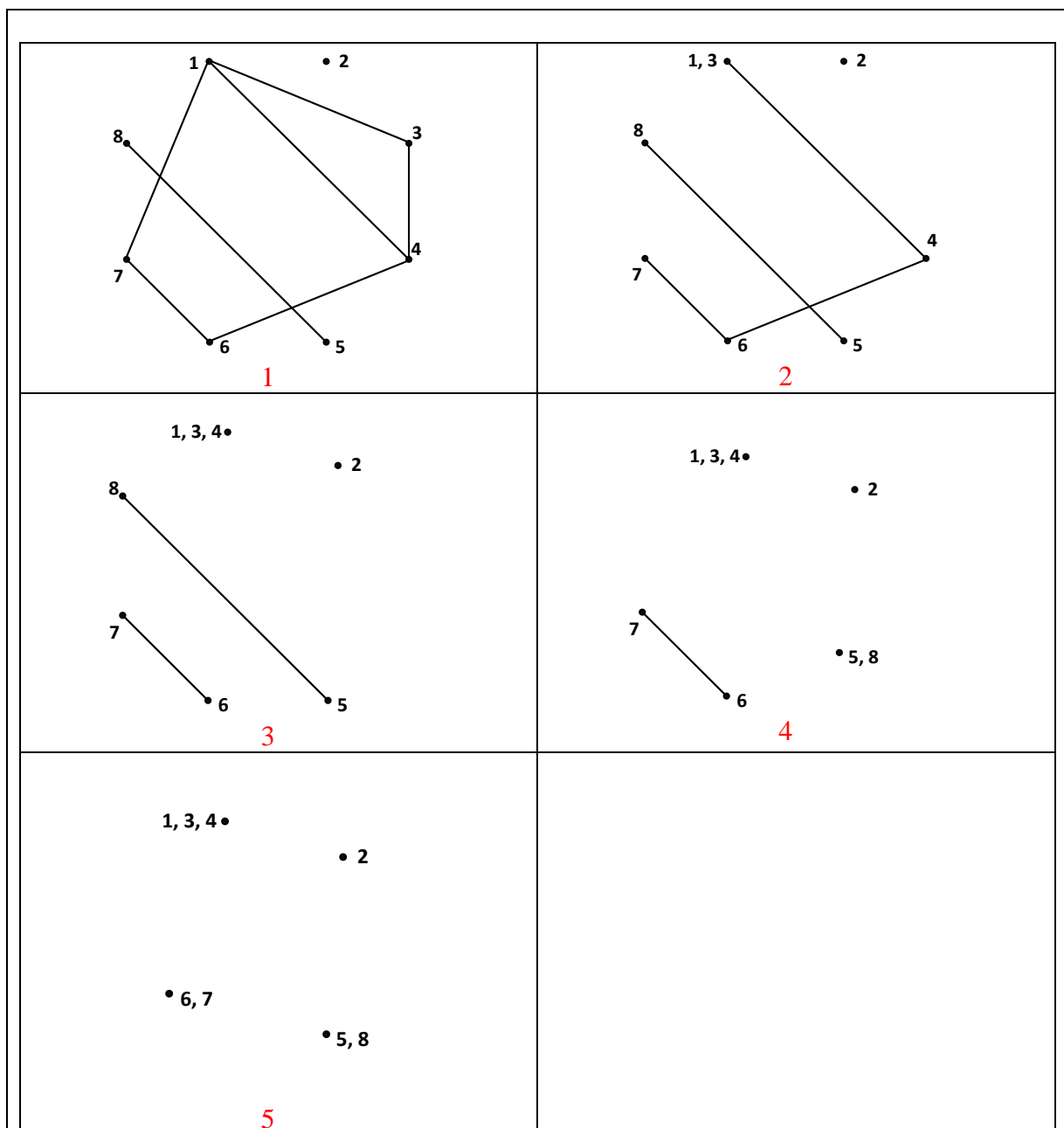

Solutions to Classwork #10 #15

Diagnosis + Compression

Problem 5 PODEM-X <video 15.1> (self-practice)

Please redo problem 2 using PODEM-X, while swap the primary and the secondary fault.
(Primary fault f SA0, secondary fault g SA0)

Primary Fault: f SA0

Initial objective: $f = 1$

Backtrace to PI: $a = 1$


Implication: $f = D$

Objective: $i_1 = 1$

Backtrace to PI: $b = 1$

Implication: $i = i_1 = i_2 = 1, k = D, m = 0$

Test cube: $abcde = 1\ 1\ x\ x\ x$

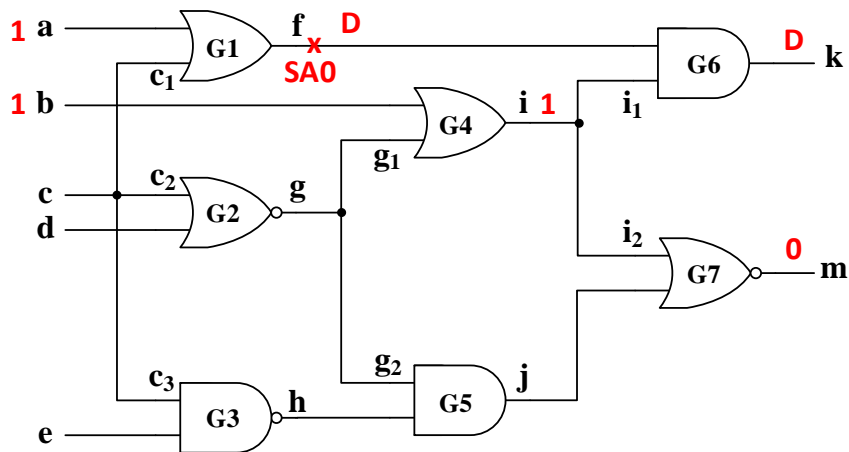

Since there is no $PO = X$, we cannot target the secondary fault.